

Lecture 8

Chapter 13

Magnetically Coupled Circuits

Md. Omar Faruque

Lecturer

Department of Electrical and Electronic Engineering

City University

Email – write2faruque@gmail.com

Mutual Inductance

When two inductors (or coils) are in a close proximity to each other, the magnetic flux caused by current in one coil links with the other coil, thereby inducing voltage in the latter. This phenomenon is known as *mutual inductance*.

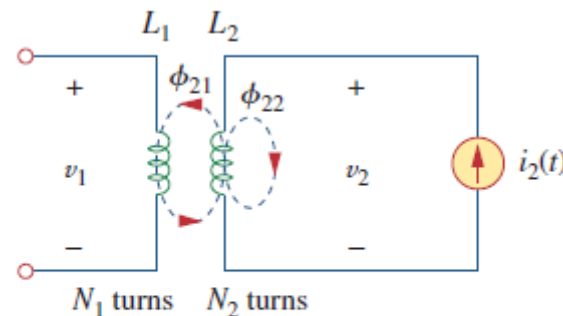


Figure 13.3
Mutual inductance M_{12} of coil 1 with respect to coil 2.

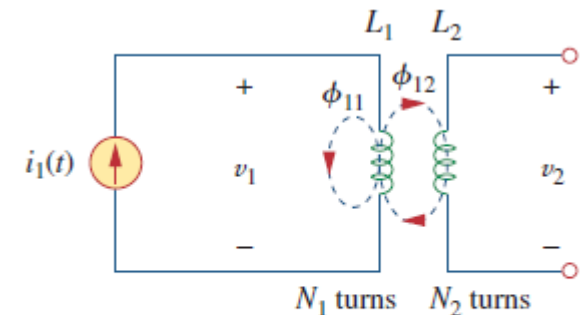


Figure 13.2
Mutual inductance M_{21} of coil 2 with respect to coil 1.

open-circuit *mutual voltage*

$$v_1 = M_{12} \frac{di_2}{dt}$$

$$v_2 = M_{21} \frac{di_1}{dt}$$

$$M_{12} = M_{21} = M \quad (13.17)$$

and we refer to M as the mutual inductance between the two coils. Like self-inductance L , mutual inductance M is measured in henrys (H).

Dot Convention

The dots are used along with the dot convention to determine the polarity of the mutual voltage. The dot convention is stated as follows:

If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.

Alternatively,

If a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.

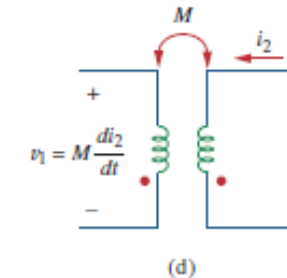
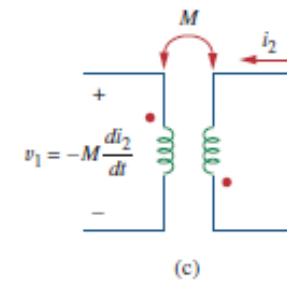
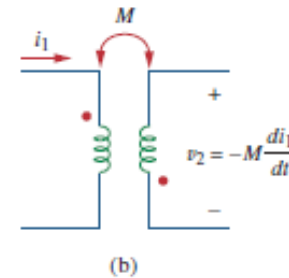
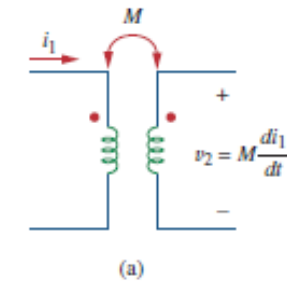


Figure 13.5
Examples illustrating how to apply the dot convention.

Analysis of mutually coupled Circuits

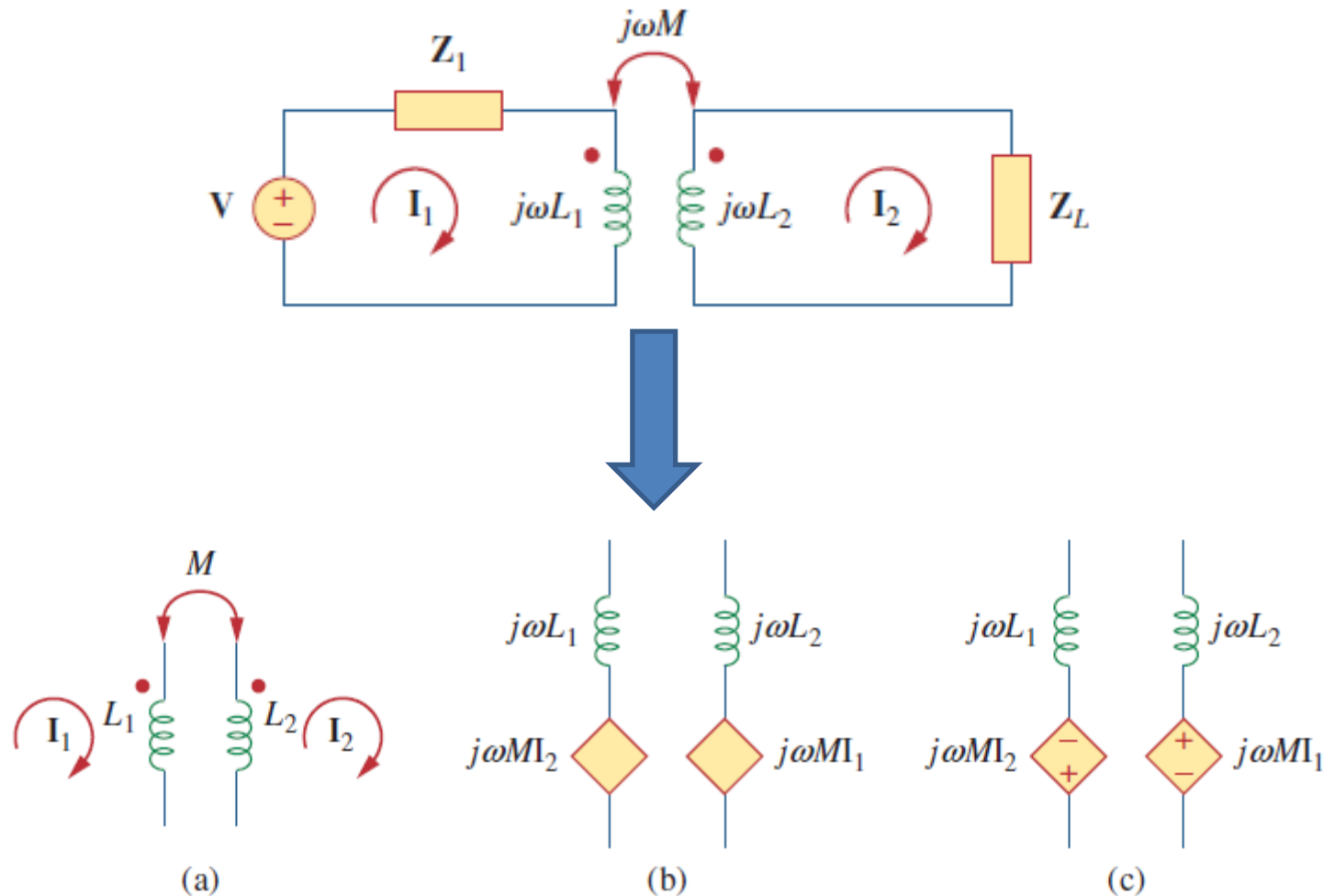




Figure 13.8

Model that makes analysis of mutually coupled easier to solve.

MATH

Calculate the phasor currents \mathbf{I}_1 and \mathbf{I}_2 in the circuit of Fig. 13.9.

Example 13.1

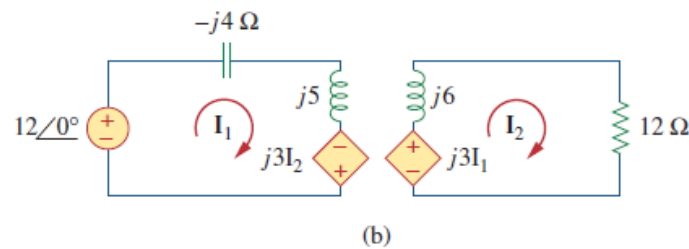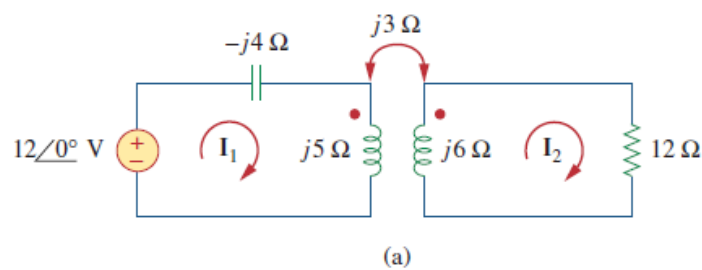

Simplified circuit

Solution:

For loop 1, KVL gives

$$-12 + (-j4 + j5)\mathbf{I}_1 - j3\mathbf{I}_2 = 0$$

or

$$j\mathbf{I}_1 - j3\mathbf{I}_2 = 12 \quad (13.1.1)$$

For loop 2, KVL gives

$$-j3\mathbf{I}_1 + (12 + j6)\mathbf{I}_2 = 0$$

or

$$\mathbf{I}_1 = \frac{(12 + j6)\mathbf{I}_2}{j3} = (2 - j4)\mathbf{I}_2 \quad (13.1.2)$$

Substituting this in Eq. (13.1.1), we get

$$(j2 + 4 - j3)\mathbf{I}_2 = (4 - j)\mathbf{I}_2 = 12$$

or

$$\mathbf{I}_2 = \frac{12}{4 - j} = 2.91 \angle 14.04^\circ \text{ A} \quad (13.1.3)$$

From Eqs. (13.1.2) and (13.1.3),

$$\begin{aligned} \mathbf{I}_1 &= (2 - j4)\mathbf{I}_2 = (4.472 \angle -63.43^\circ)(2.91 \angle 14.04^\circ) \\ &= 13.01 \angle -49.39^\circ \text{ A} \end{aligned}$$

H.W
Practice problem
13.1

Linear transformer

A **transformer** is generally a four-terminal device comprising two (or more) magnetically coupled coils.

A **linear transformer** may also be regarded as one whose flux is proportional to the currents in its windings.

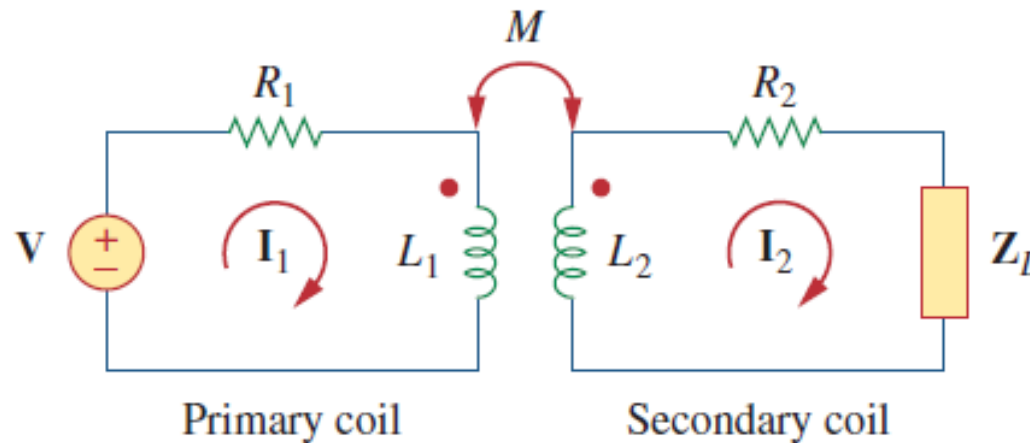


Figure 13.19
A linear transformer.

Equivalent circuit of a Linear Transformer

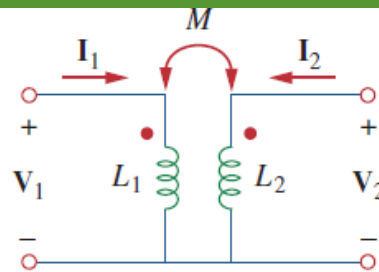


Figure 13.21

Determining the equivalent circuit of a linear transformer.

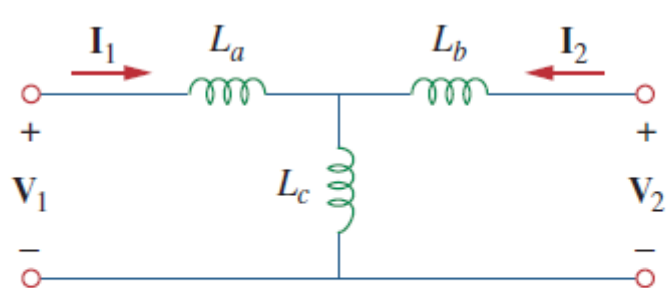


Figure 13.22

An equivalent T circuit.

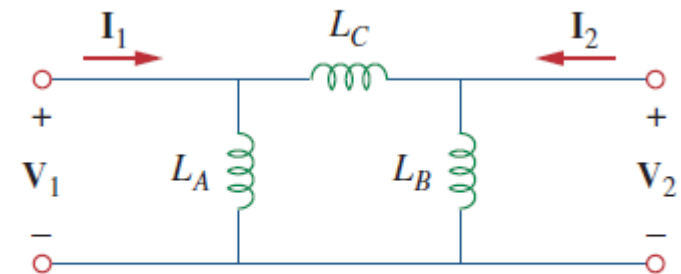
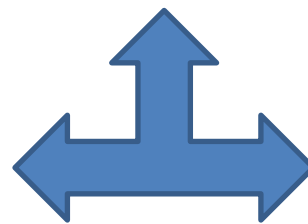


Figure 13.23

An equivalent Π circuit.

$$L_a = L_1 - M, \quad L_b = L_2 - M, \quad L_c = M$$

$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M}, \quad L_B = \frac{L_1 L_2 - M^2}{L_1 - M}$$

$$L_C = \frac{L_1 L_2 - M^2}{M}$$

MATH

Determine the T-equivalent circuit of the linear transformer in Fig. 13.26(a).

Example 13.5

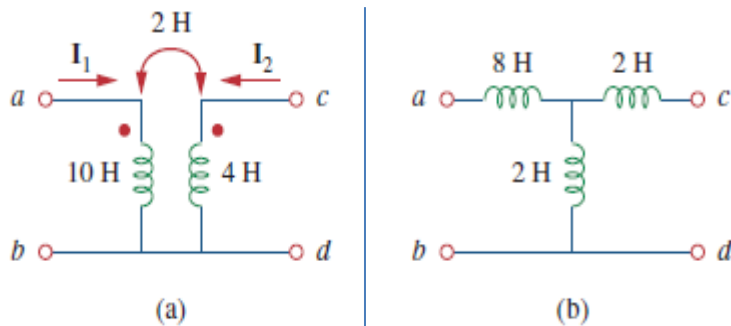


Figure 13.26

For Example 13.5: (a) a linear transformer, (b) its T-equivalent circuit.

Solution:

Given that $L_1 = 10$, $L_2 = 4$, and $M = 2$, the T-equivalent network has the following parameters:

$$L_a = L_1 - M = 10 - 2 = 8 \text{ H}$$

$$L_b = L_2 - M = 4 - 2 = 2 \text{ H}, \quad L_c = M = 2 \text{ H}$$

H.W
Practice problem
13.5

H.W
Example
13.6