

Lecture 6

Chapter 12

Three-Phase Circuits

Md. Omar Faruque

Lecturer

Department of Electrical and Electronic Engineering


City University

Email – write2faruque@gmail.com

1-phase System



(a) two-wire type

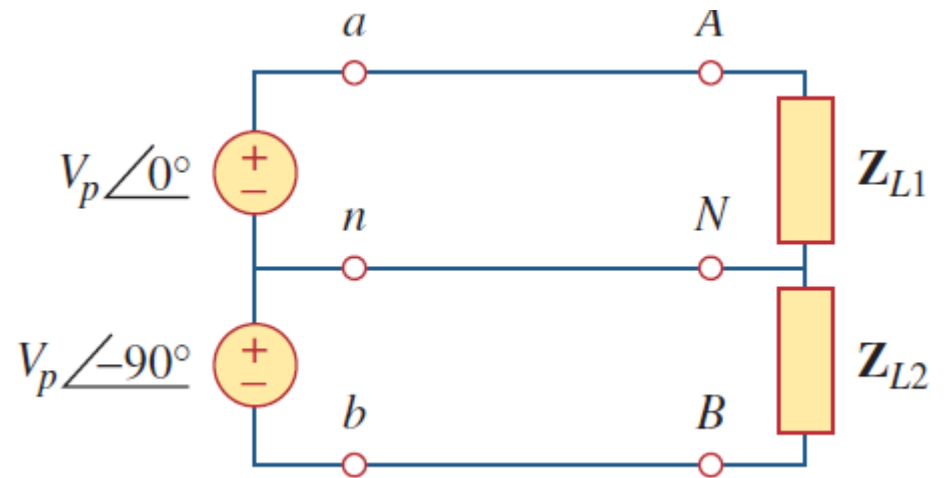

(b) three-wire type.

3-phase system

Why 3-phase system?

- **First, nearly all electric power is generated and distributed in three-phase.**
When one-phase or two-phase inputs are required, they are taken from the three-phase system rather than generated independently.
- **Second, the instantaneous power in a three-phase system can be constant (not pulsating)**
- **Third, for the same amount of power, the three-phase system is more economical than the single phase.**
The amount of wire required for a three-phase system is less than that required for an equivalent single-phase system.

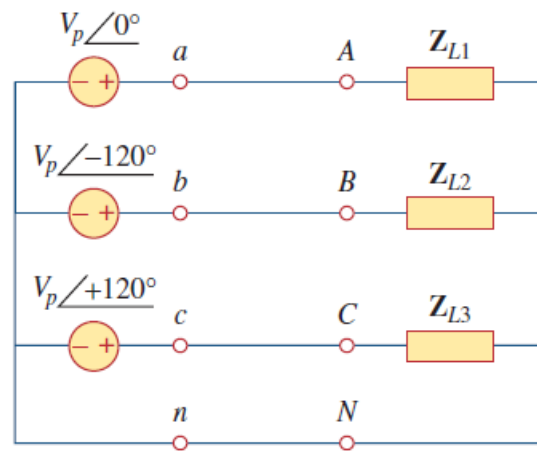


Figure 12.3
Three-phase four-wire system.

Balanced 3-phase system

Balanced phase voltages are equal in magnitude and are out of phase with each other by 120.

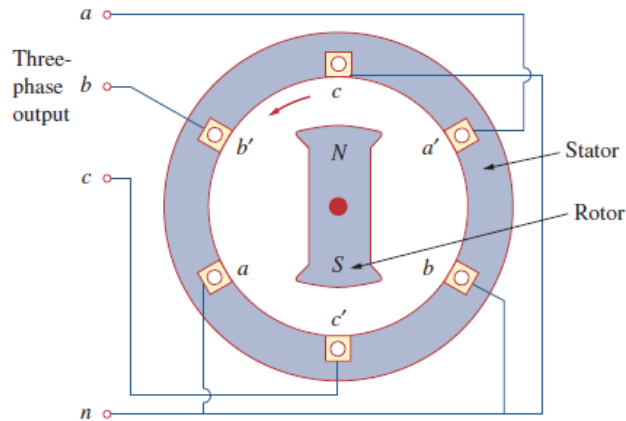


Figure 12.4
A three-phase generator.

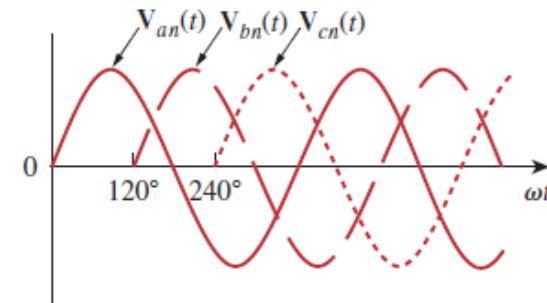


Figure 12.5
The generated voltages are 120° apart from each other.


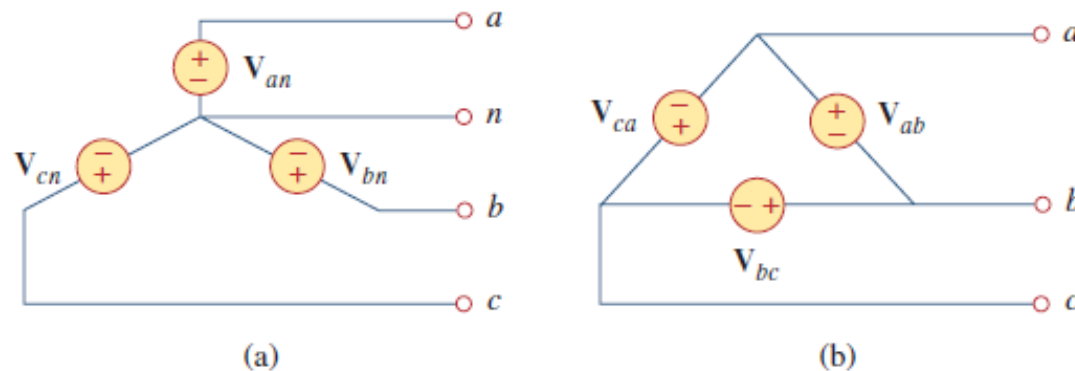


Figure 12.6
Three-phase voltage sources: (a) Y-connected source, (b) Δ -connected source.


Phase Sequence

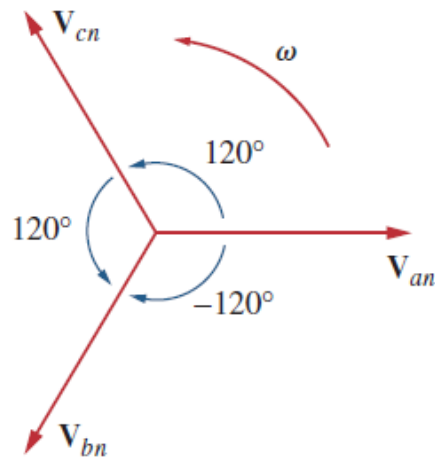The phase sequence is the time order in which the voltages pass through their respective maximum values.



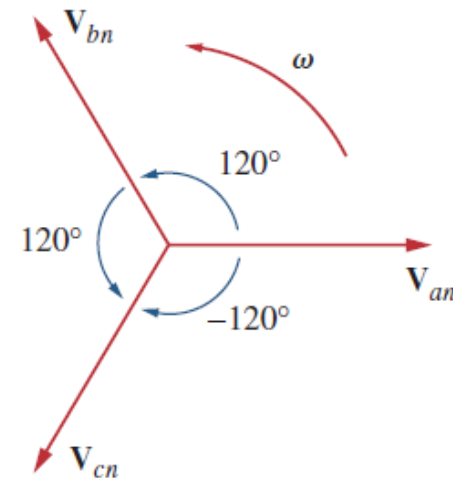(a) *abc* or positive

$$\begin{aligned} \mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{bn} &= V_p \angle -120^\circ \\ \mathbf{V}_{cn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$



(b) *acb* or negative sequence.

$$\begin{aligned} \mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{cn} &= V_p \angle -120^\circ \\ \mathbf{V}_{bn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} &= V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle +120^\circ \\ &= V_p(1.0 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= 0 \end{aligned}$$

Balanced 3-phase load

A **balanced load** is one in which the phase impedances are equal in magnitude and in phase.

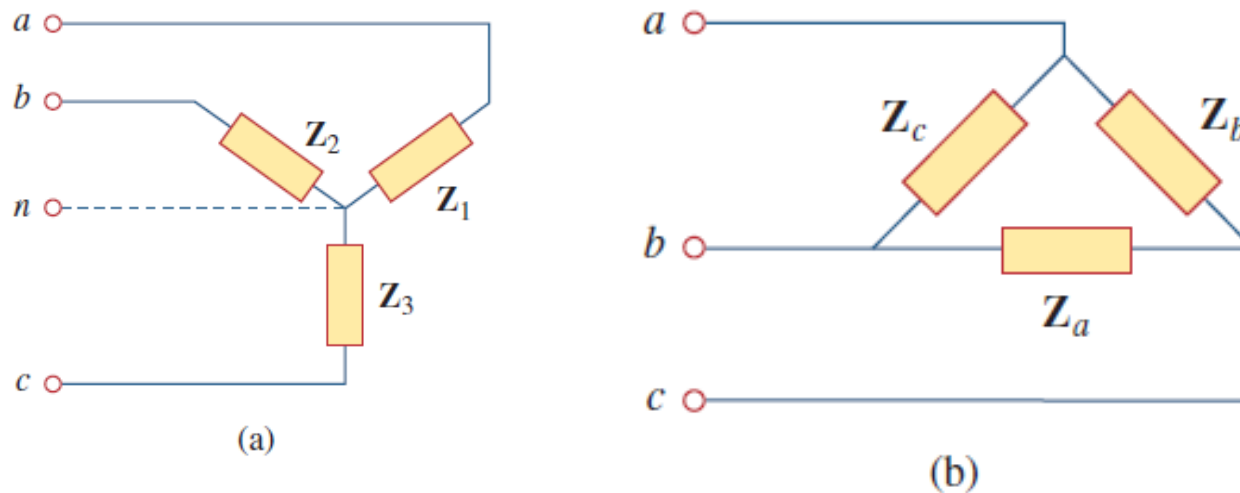


Figure 12.8

Two possible three-phase load configurations: (a) a Y-connected load, (b) a Δ -connected load.

For a *balanced* wye-connected load,

$$Z_1 = Z_2 = Z_3 = Z_Y \quad (12.6)$$

where Z_Y is the load impedance per phase. For a *balanced* delta-connected load,

$$Z_a = Z_b = Z_c = Z_\Delta \quad (12.7)$$

where Z_Δ is the load impedance per phase in this case. We recall from Eq. (9.69) that





$$Z_\Delta = 3Z_Y \quad \text{or} \quad Z_Y = \frac{1}{3}Z_\Delta \quad (12.8)$$

so we know that a wye-connected load can be transformed into a delta-connected load, or vice versa, using Eq. (12.8).

3-phase connections

Since both the three-phase source and the three-phase load can be either wye- or delta-connected, we have four possible connections:

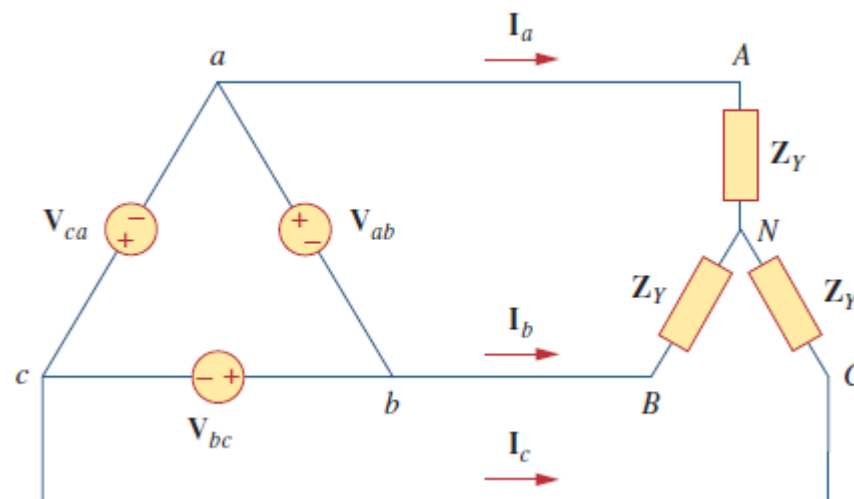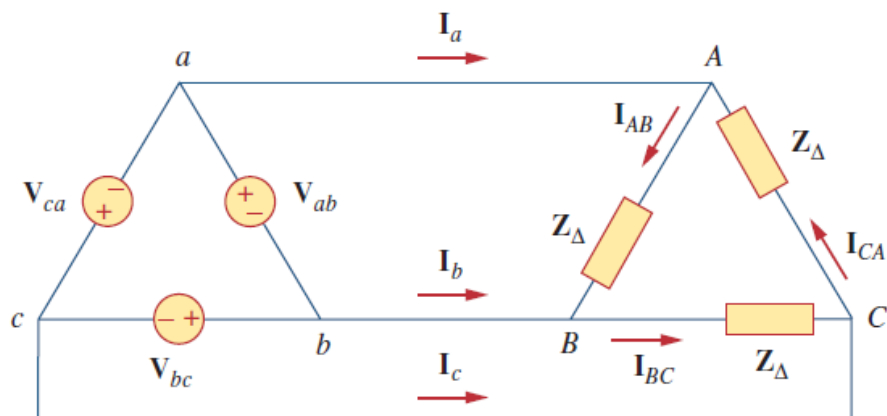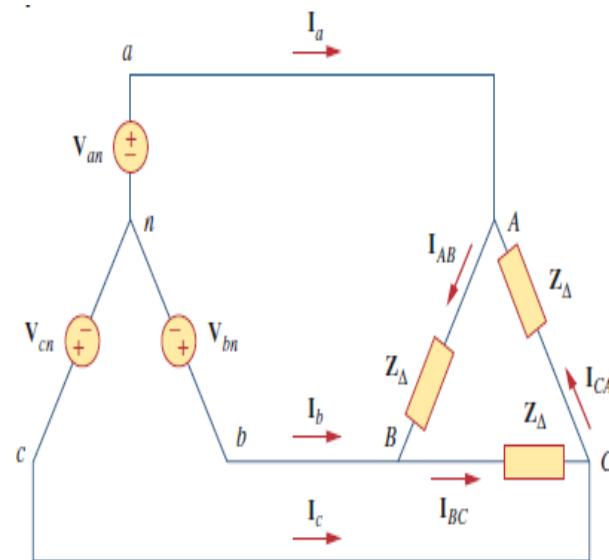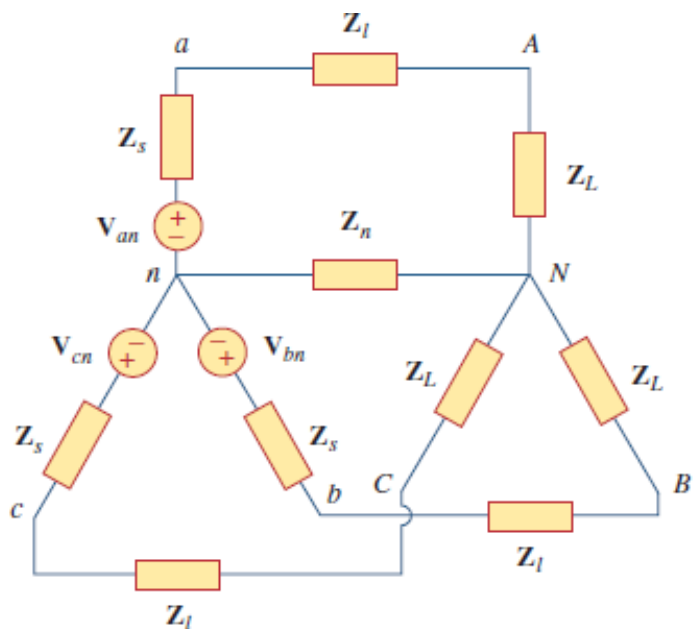- Y-Y connection (i.e., Y-connected source with a Y-connected load).
- Y- Δ connection.
- Δ - Δ connection.
- Δ -Y connection.



Balanced Y-Y System

A balanced Y-Y system is a three-phase system with a balanced Y-connected source and a balanced Y-connected load.

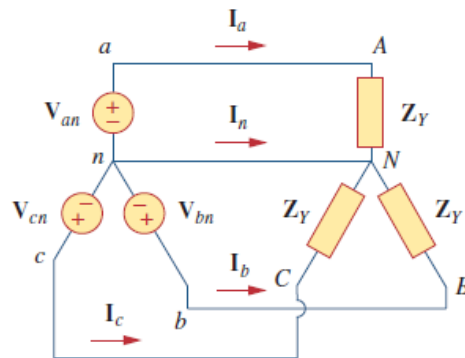


Figure 12.10
Balanced Y-Y connection.

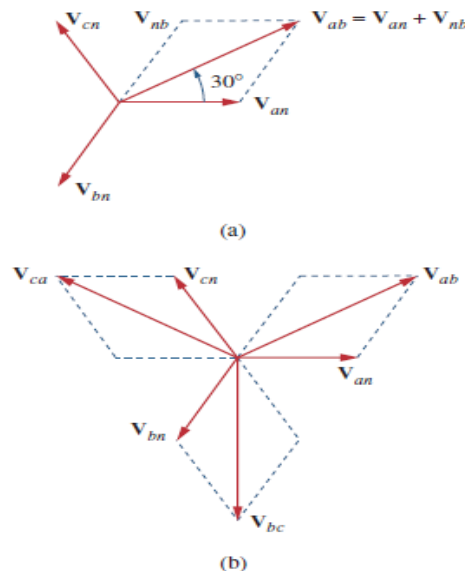


Figure 12.11
Phasor diagrams illustrating the relationship between line voltages and phase voltages.

Assuming the positive sequence, the *phase* voltages (or line-to-neutral voltages) are

$$V_{an} = V_p \angle 0^\circ \quad (12.10)$$

$$V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

The *line-to-line* voltages or simply *line* voltages V_{ab} , V_{bc} , and V_{ca} are related to the phase voltages. For example,

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left(1 + \frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \end{aligned} \quad (12.11a)$$

Similarly, we can obtain

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ \quad (12.11b)$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ \quad (12.11c)$$

Thus, the magnitude of the line voltages V_L is $\sqrt{3}$ times the magnitude of the phase voltages V_p , or

$$V_L = \sqrt{3} V_p \quad (12.12)$$

where

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}| \quad (12.13)$$

and

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}| \quad (12.14)$$

Balanced Y-Y Circuit Analysis

An alternative way of analyzing a balanced Y-Y system is to do so on a “per phase” basis. We look at one phase, say phase a , and analyze the single-phase equivalent circuit in Fig. 12.12. The single-phase analysis yields the line current \mathbf{I}_a as

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} \quad (12.18)$$

From \mathbf{I}_a , we use the phase sequence to obtain other line currents. Thus, as long as the system is balanced, we need only analyze one phase. We may do this even if the neutral line is absent, as in the three-wire system.

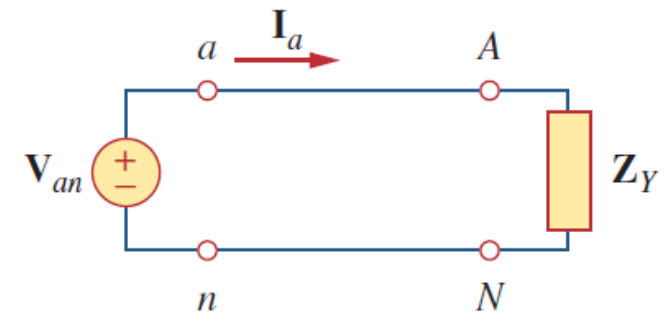


Figure 12.12

A single-phase equivalent circuit.

MATH

Example 12.2

Calculate the line currents in the three-wire Y-Y system of Fig. 12.13.

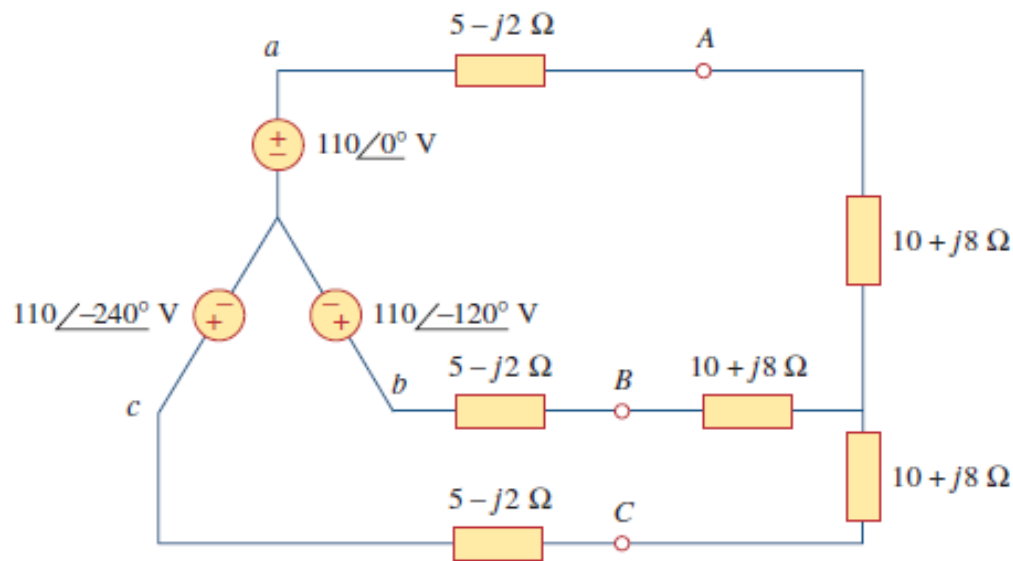


Figure 12.13

Three-wire Y-Y system; for Example 12.2.

H.W
Practice problem
12.2

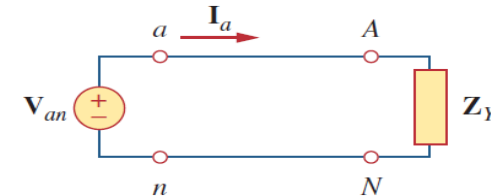


Figure 12.12

A single-phase equivalent circuit.

Solution:

The three-phase circuit in Fig. 12.13 is balanced; we may replace it with its single-phase equivalent circuit such as in Fig. 12.12. We obtain I_a from the single-phase analysis as

$$I_a = \frac{V_{an}}{Z_Y}$$

where $Z_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155\angle 21.8^\circ$. Hence,

$$I_a = \frac{110\angle 0^\circ}{16.155\angle 21.8^\circ} = 6.81\angle -21.8^\circ \text{ A}$$

Since the source voltages in Fig. 12.13 are in positive sequence, the line currents are also in positive sequence:

$$I_b = I_a\angle -120^\circ = 6.81\angle -141.8^\circ \text{ A}$$

$$I_c = I_a\angle -240^\circ = 6.81\angle -261.8^\circ \text{ A} = 6.81\angle 98.2^\circ \text{ A}$$

Balanced Y-Δ System

A balanced Y- Δ system consists of a balanced Y-connected source feeding a balanced Δ connected load.

example, applying KVL around loop $aABbna$ gives

$$-V_{an} + Z_{\Delta}I_{AB} + V_{bn} = 0$$

or

$$I_{AB} = \frac{V_{an} - V_{bn}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}} = \frac{V_{AB}}{Z_{\Delta}} \quad (12.22)$$

which is the same as Eq. (12.21). This is the more general way of finding the phase currents.

The line currents are obtained from the phase currents by applying KCL at nodes A, B, and C. Thus,

$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC} \quad (12.23)$$

Since $I_{CA} = I_{AB} \angle -240^\circ$,

$$\begin{aligned} I_a &= I_{AB} - I_{CA} = I_{AB}(1 - 1 \angle -240^\circ) \\ &= I_{AB}(1 + 0.5 - j0.866) = I_{AB}\sqrt{3} \angle -30^\circ \end{aligned} \quad (12.24)$$

showing that the magnitude I_L of the line current is $\sqrt{3}$ times the magnitude I_p of the phase current, or


$$I_L = \sqrt{3}I_p \quad (12.25)$$

where

$$I_L = |I_a| = |I_b| = |I_c| \quad (12.26)$$

and

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}| \quad (12.27)$$

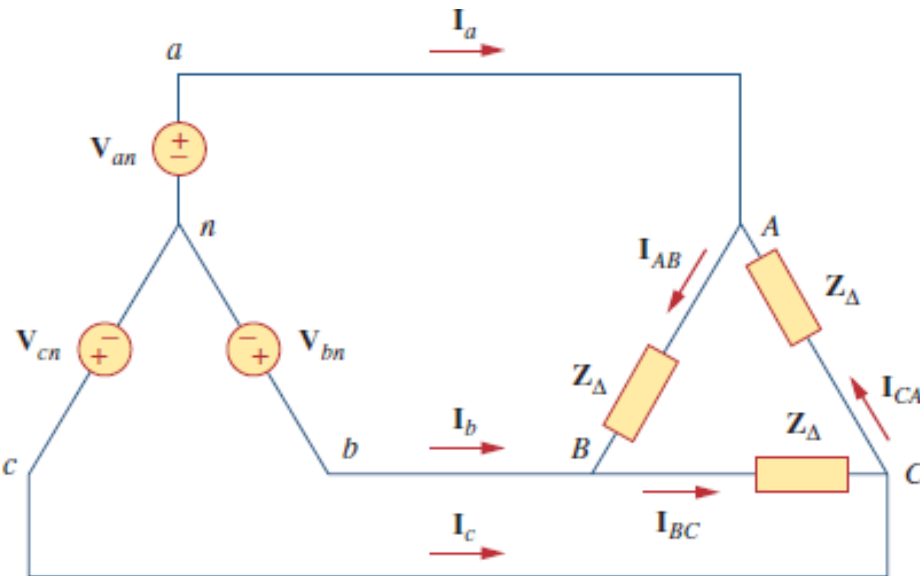

Y-Δ System Circuit Analysis

An alternative way of analyzing the Y-Δ circuit is to transform the Δ-connected load to an equivalent Y-connected load. Using the Δ-Y transformation formula in Eq. (12.8),

$$Z_Y = \frac{Z_{\Delta}}{3} \quad (12.28)$$

After this transformation, we now have a Y-Y system as in Fig. 12.10. The three-phase Y-Δ system in Fig. 12.14 can be replaced by the single-phase equivalent circuit in Fig. 12.16. This allows us to calculate only the line currents. The phase currents are obtained using Eq. (12.25) and utilizing the fact that each of the phase currents leads the corresponding line current by 30° .

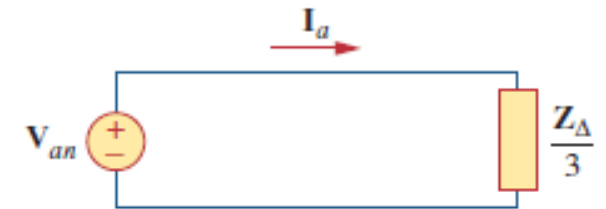



Figure 12.16

A single-phase equivalent circuit of a balanced Y-Δ circuit.

MATH

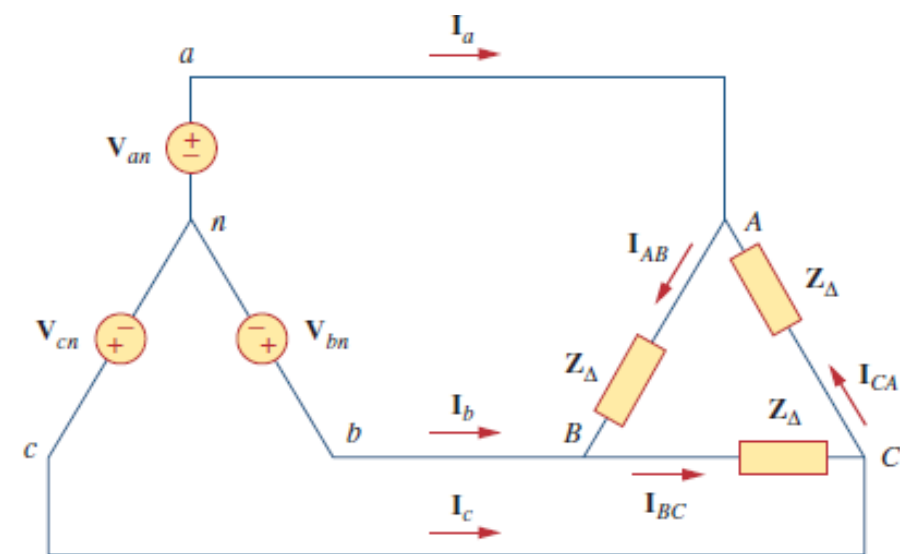Example 12.3

A balanced abc -sequence Y-connected source with $V_{an} = 100\angle 10^\circ$ V is connected to a Δ -connected balanced load $(8 + j4) \Omega$ per phase. Calculate the phase and line currents.



H.W
Practice problem
12.3,12.4,12.5

Solution:

This can be solved in two ways.

METHOD 1

The load impedance is

$$Z_{\Delta} = 8 + j4 = 8.944\angle 26.57^\circ \Omega$$

If the phase voltage $V_{an} = 100\angle 10^\circ$, then the line voltage is

$$V_{ab} = V_{an}\sqrt{3}\angle 30^\circ = 100\sqrt{3}\angle 10^\circ + 30^\circ = V_{AB}$$

or

$$V_{AB} = 173.2\angle 40^\circ \text{ V}$$

The phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{173.2\angle 40^\circ}{8.944\angle 26.57^\circ} = 19.36\angle 13.43^\circ \text{ A}$$

$$I_{BC} = I_{AB}\angle -120^\circ = 19.36\angle -106.57^\circ \text{ A}$$

$$I_{CA} = I_{AB}\angle +120^\circ = 19.36\angle 133.43^\circ \text{ A}$$

The line currents are

$$I_a = I_{AB}\sqrt{3}\angle -30^\circ = \sqrt{3}(19.36)\angle 13.43^\circ - 30^\circ = 33.53\angle -16.57^\circ \text{ A}$$

$$I_b = I_a\angle -120^\circ = 33.53\angle -136.57^\circ \text{ A}$$

$$I_c = I_a\angle +120^\circ = 33.53\angle 103.43^\circ \text{ A}$$

METHOD 2

Alternatively, using single-phase analysis,

$$I_a = \frac{V_{an}}{Z_{\Delta}/3} = \frac{100\angle 10^\circ}{2.981\angle 26.57^\circ} = 33.54\angle -16.57^\circ \text{ A}$$

as above. Other line currents are obtained using the abc phase sequence.

Balanced 3-phase System Summary

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Same as line currents	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{an} / Z_Y$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y-Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB} / Z_\Delta$ $I_{BC} = V_{BC} / Z_\Delta$ $I_{CA} = V_{CA} / Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = V_{ab} / Z_\Delta$ $I_{BC} = V_{bc} / Z_\Delta$ $I_{CA} = V_{ca} / Z_\Delta$	Same as phase voltages $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

Unbalanced 3-phase System

An unbalanced system is due to unbalanced voltage sources or an unbalanced load.

- Unbalanced three-phase systems are solved by direct application of mesh and nodal analysis.

Example 12.9

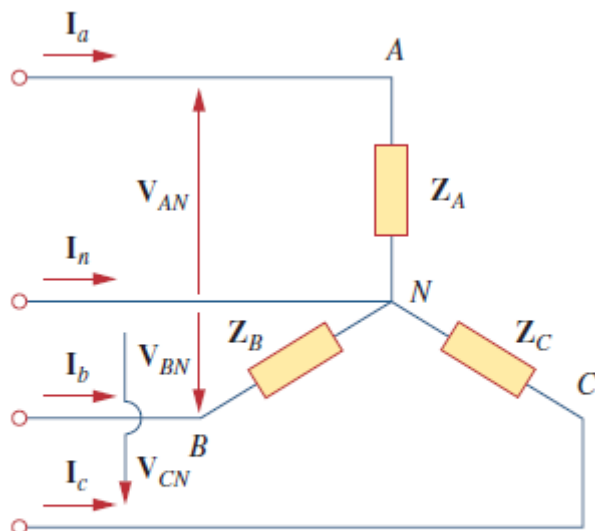


Figure 12.23

Unbalanced three-phase Y-connected load

$$I_a = \frac{V_{AN}}{Z_A}, \quad I_b = \frac{V_{BN}}{Z_B}, \quad I_c = \frac{V_{CN}}{Z_C}$$

$$I_n = -(I_a + I_b + I_c)$$

The unbalanced Y-load of Fig. 12.23 has balanced voltages of 100 V and the *acb* sequence. Calculate the line currents and the neutral current. Take $Z_A = 15 \Omega$, $Z_B = 10 + j5 \Omega$, $Z_C = 6 - j8 \Omega$.

Solution:

Using Eq. (12.59), the line currents are

$$I_a = \frac{100 \angle 0^\circ}{15} = 6.67 \angle 0^\circ \text{ A}$$

$$I_b = \frac{100 \angle 120^\circ}{10 + j5} = \frac{100 \angle 120^\circ}{11.18 \angle 26.56^\circ} = 8.94 \angle 93.44^\circ \text{ A}$$

$$I_c = \frac{100 \angle -120^\circ}{6 - j8} = \frac{100 \angle -120^\circ}{10 \angle -53.13^\circ} = 10 \angle -66.87^\circ \text{ A}$$

Using Eq. (12.60), the current in the neutral line is

$$I_n = -(I_a + I_b + I_c) = -(6.67 - 0.54 + j8.92 + 3.93 - j9.2) \\ = -10.06 + j0.28 = 10.06 \angle 178.4^\circ \text{ A}$$

H.W

Practice problem 12.9